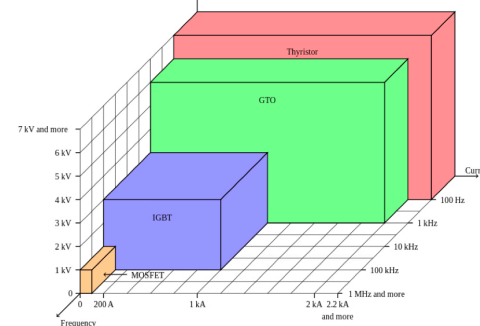


	Buck	Boost	Buck-Boost
$\frac{\langle v_o \rangle}{V_i}$	D	$\frac{1}{1-D}$	$\frac{D}{1-D}$
L_{crit}	$\frac{V_i - \langle v_o \rangle}{2 \langle v_o \rangle} RDT$	$\frac{V_i^2}{2 \langle v_o \rangle^2} RDT$	$\frac{V_i^2 / (V_i + \langle v_o \rangle)}{2 \langle v_o \rangle} RDT$
C	$\frac{T \Delta i_L}{8 \Delta V_o}$	$\langle v_o \rangle \frac{DT}{R \Delta V_o}$	$\langle v_o \rangle \frac{DT}{R \Delta V_o}$
DCM: $\frac{\langle v_o \rangle}{V_i}$	$\frac{RD^2T}{4L} + D \sqrt{\frac{RT}{2L} + \frac{R^2 D^2 T^2}{16 L^2}}$	$\frac{1}{2} + \sqrt{\frac{1}{4} + \frac{RD^2T}{2L}}$	$D \sqrt{\frac{RT}{2L}}$

	Thyristor	GTO	BJT	MOSFET	IGBT
Availability	Early 60s	Mid 80s	Late 70s	Early 80s	Late 80s
Drive Circuit	Simple	Very difficult	Difficult	Very simple	Very simple
Trait	Can't turn off using gate signals	King in very high power	Phasing out in new products	Good performance in high frequency	Best of all performance





Comparison

Review!

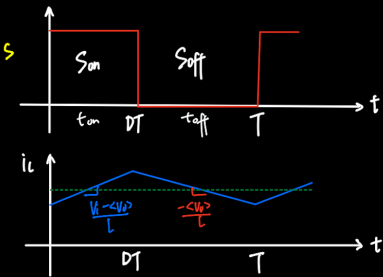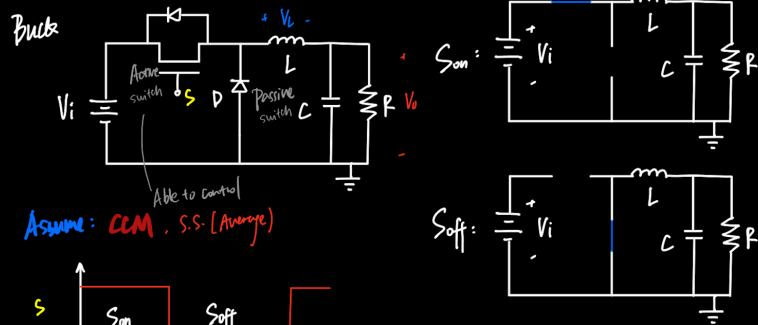6. Buck Converters

Buck Converter Operation and Voltage Equation



$$\frac{V_i - \langle V_o \rangle}{L} DT = \frac{\langle V_o \rangle}{L} (1-D)T$$

$$(V_i - \langle V_o \rangle)D = \langle V_o \rangle(1-D)$$



$$DV_i - D\langle V_o \rangle = \langle V_o \rangle - D\langle V_o \rangle$$

$$DV_i = \langle V_o \rangle$$

$$D = \frac{\langle V_o \rangle}{V_i}$$

Boost Converters

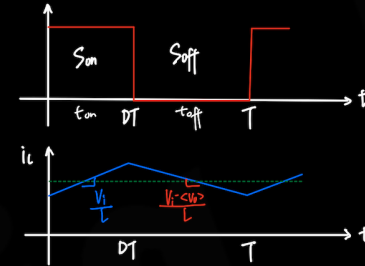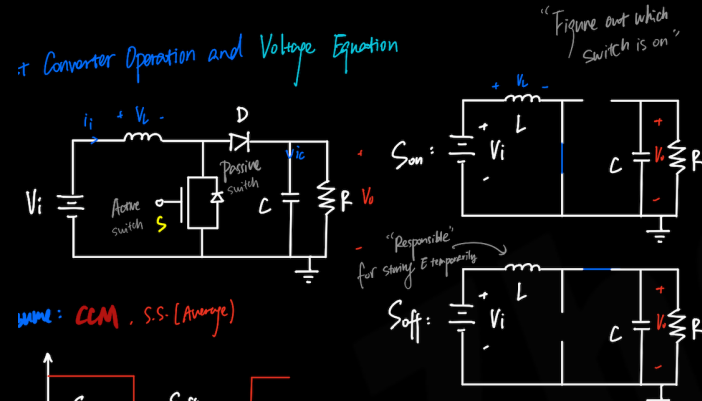Boost Converter Operation and Voltage Equation



$$\Delta i_L = \frac{V_i}{L} DT + \frac{V_i - \langle V_o \rangle}{L} (1-D)T = 0$$

$$\Rightarrow V_i D = (V_i + \langle V_o \rangle)(1-D)$$



$$V_i D = V_i D - V_i + \langle V_o \rangle - \langle V_o \rangle D$$

$$V_i = \langle V_o \rangle (1-D)$$


$$\langle V_o \rangle = V_i \frac{1}{1-D}$$

inverts

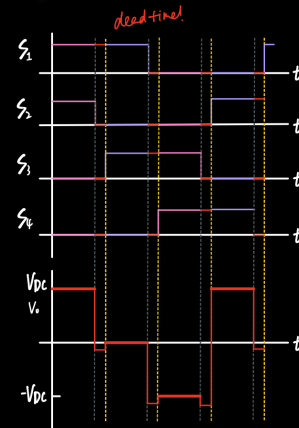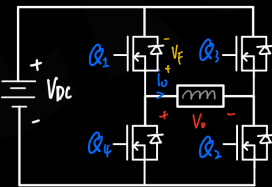Half-Bridge Inverter with MOSFET Switches



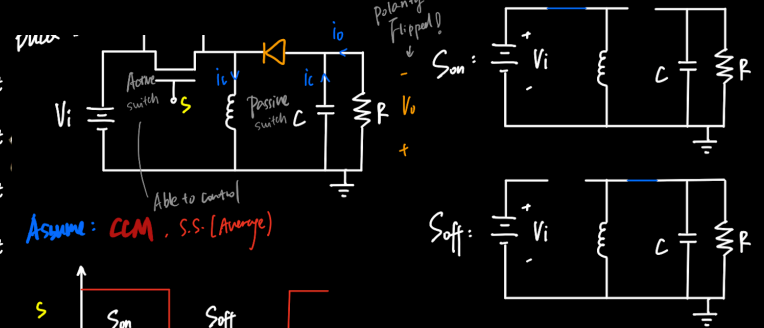Half-Bridge Inverter Operation and Voltage Equation



$$\Delta i_L = \frac{V_i}{L} DT + \frac{-\langle V_o \rangle}{L} (1-D)T = 0$$


$$\Rightarrow V_i D = \langle V_o \rangle (1-D)$$

$$V_i = \langle V_o \rangle \frac{1-D}{D}$$

$$\langle V_o \rangle = V_i \frac{D}{1-D}$$

11. Full-Bridge Inverters

Half-Bridge Inverter Switch States

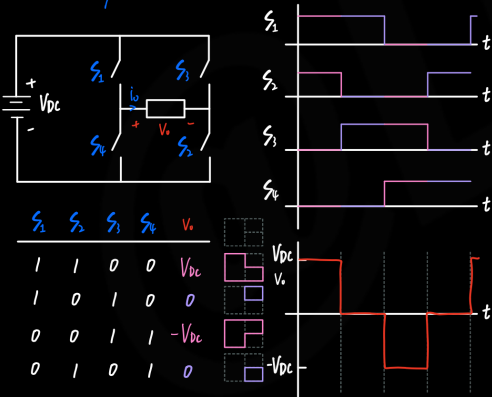

	Q_1	Q_2	Q_3	Q_4	V_o
V_F	1	1	0	0	V_{dc}
$V_{dc} + V_F$	1	0	0	0	$-V_F \text{ for } V_{dc} + V_F$
$-V_F$	0	0	1	0	$-V_{dc} - V_F \text{ for } -V_F$
$-V_{dc} - V_F$	0	0	1	1	$-V_{dc}$
or	0	0	0	1	$-V_{dc} - V_F \text{ for } -V_F$
	0	1	0	1	0
	0	1	0	0	$0 - V_F \text{ for } V_{dc} + V_F$